
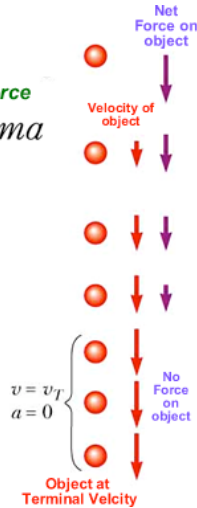


A Mechanical Analog

An object falling through a liquid reaches terminal velocity due to two competing forces.

$$\Sigma F = mg - bv = ma$$

Viscous Force
Gravitational Force

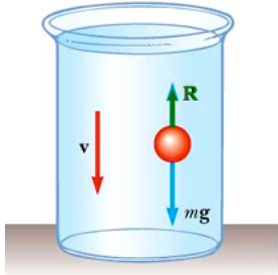

Sum of the Forces

$$\Sigma F = mg - bv = ma$$

Separate Variables

$$\frac{dv}{g - \frac{b}{m}v} = dt$$

Integrate

2 pts

Solve for the acceleration

$$g - \frac{b}{m}v = a = \frac{dv}{dt}$$

$$\int_0^v \frac{dv}{g - \frac{b}{m}v} = \int_0^t dt$$

$$(g - \frac{b}{m}v)/g = e^{-bt/m}$$

Solve for Velocity


2 pts

Physics 196 Chapter 31 Problem 66


The bar of mass m in is pulled horizontally across parallel rails by a massless string that passes over an ideal pulley and is attached to a suspended mass M . The uniform magnetic field has a magnitude B , and the distance between the rails is ℓ . The rails are connected at one end by a load resistor R . Derive an expression that gives the horizontal speed of the bar as a function of time.

Draw Induced current, Magnetic Field and Mag-Force.

2 pts

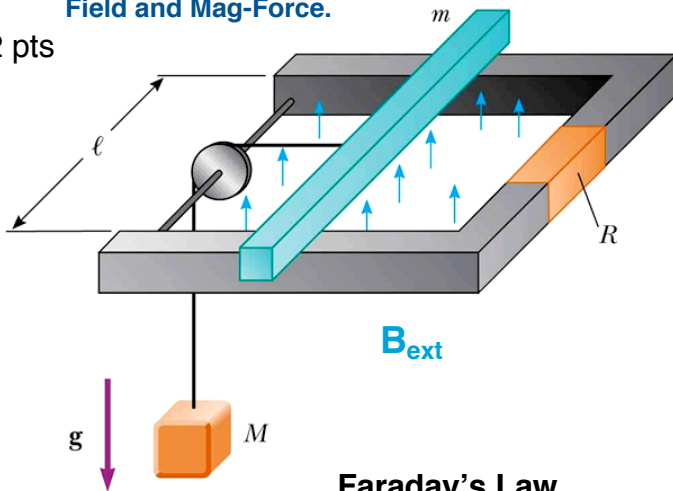

FreeBody Diagrams

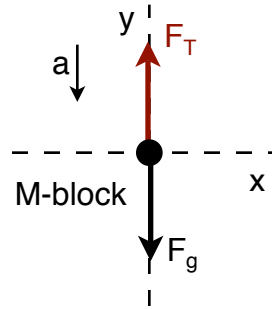

3 pts

Faraday's Law

1 pts

The *magnetic flux is changing* through the area bounded by the bar and the rails. According to **Faraday's Law** a *changing magnetic flux* will induce an **emf** in the circuit which will then produce a **current** which will then produce an **induced magnetic field** that will **oppose** the *changing magnetic flux*.

Looking at the diagram, the direction of the induced current is counterclockwise. This will produce a **magnetic field** that will add to the external magnetic field through the circuit. Since the arrows are pointing in the same direction there is a *repulsion* between the **induced** and the **external** magnetic fields to the right.

Since the magnetic flux is decreasing through the circuit the induced magnetic field will produce a force on the bar that will **oppose** this change.

Sum of the Forces

$$\Sigma F_y = F_T - F_g = -Ma_y$$

1 pts

Falling Mass

$$a_y = a_x$$

Sliding Bar

$$F_T = mg - Ma$$

1 pts

We need to find the **induced magnetic force**

$$\Phi_B = BA \cos \theta$$

$$I_{ind} = \frac{\epsilon}{R} =$$

2 pts

$$F_B = BI_{ind}L =$$

2 pts

Set eq's equal and solve for the acceleration

2 pts

$$\frac{mg - F_B}{M + m} = a$$

$$\frac{mg - F_B}{M + m} = \frac{dv}{dt}$$

Plug in F_B and simplify.

2 pts

Let's reduce our stress and set

$$\alpha = \frac{mg}{M + m}$$

$$\beta = \frac{B^2 l^2}{R(M + m)}$$

Separate Variables

2 pts

Draw the graph of the velocity wrt time. What is the terminal velocity? Show on the graph the velocity at e^{-2} ?

4 pts



Integrate

$$\int_0^v \frac{dv}{\alpha - \beta v} = \int_0^t dt$$

2 pts


$$(\alpha - \beta v)/\alpha = e^{-\beta t}$$

Solve for Velocity

2 pts

Physics 196 Chapter 32 Problem 71


The emf = 14.0 V, $R_1 = 2.80$ kohms, and $R_2 = 5.00$ kohms. The switch is closed for $t < 0$, and steady-state conditions are established. The switch is now thrown open at $t = 0$. (a) Find the initial voltage emf_0 across L just after $t = 0$. Which end of the coil is at the higher potential: a or b? (b) Make freehand graphs of the currents in R_1 and in R_2 as a function of time. Show values before and after $t = 0$. (c) How long after $t = 0$ does the current in R_2 have the value 2.00 mA? (30 points)

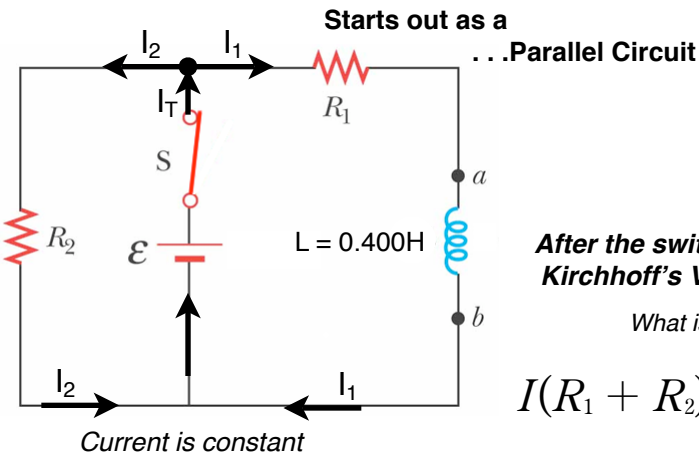

... then ends as a

Show which end of the inductor is at a higher potential. 4 pts

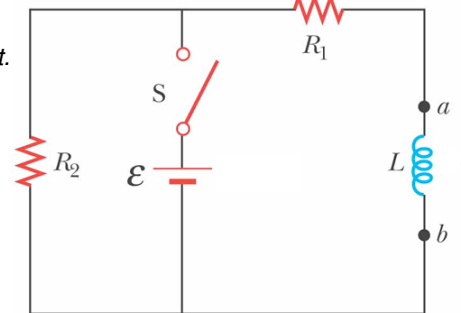Show the initial direction of the current.



Is the initial current increasing or decreasing? 3 pts

After the switch is opened use Kirchhoff's Voltage Sum Rule

What is the induced emf over the inductor?

$$I(R_1 + R_2) + \boxed{} = 0$$

Derive the current wrt time when the switch is closed.

a. The switch is closed for a long time so the current in both branches has reached a constant value.

b. The voltage over the inductor is zero because the current has stopped changing. No change in current no 'back emf'.

c. A constant Magnetic Field has been established in the coil.

Find the **steady state current** for the left and right loops when the switch is closed using Kirchhoff's Current Sum Rule.

$$I_T = I_1 + I_2$$

$$I_T = \frac{\mathcal{E}}{R_1} (1 - e^{-\frac{R_2 t}{L}}) + \frac{\mathcal{E}}{R_2}$$

Find the Steady-state current in the left and right loop

plug in values 4 pts

symbolically 6 pts

a. The power source is disconnected. Initially the current is CW / CCW thru the inductor.
 b. Because the current is _____ the coil reacts by inducing a _____ emf.
 c. The current through the inductor will begin to _____ in magnitude but continue in the _____ direction. The current in the left loop _____ direction.
 d. _____ is at a higher potential because the coil is trying to keep the current from falling to zero.

Find the initial emf over the Inductor when the switch is opened? Use Kirchhoff's Voltage Sum Rule. 2 pts

$$I = \frac{\mathcal{E}}{R_2 + R_1} (e^{-\frac{(R_2 + R_1)t}{L}})$$

$$I_f = I_0 e^{-\frac{(R_2 + R_1)t}{L}}$$

symbolically

plug in values

What is the time required for current to fall to 2.00mA?

plug in values 2 pts

Put values on the graphs below.

